

Introduction to Sequential Circuits

EIC 0844091

Digital Circuit and Logic Design

Associate Prof. Luo Jie

Huazhong University of Science & Technology

Presentation Outline

- ❖ Introduction to Sequential Circuits
- ❖ Synchronous versus Asynchronous
- ❖ Latches
- ❖ Flip-Flops
- ❖ Characteristic Tables and Equations

Combinational versus Sequential

❖ Two classes of digital circuits

- ❖ Combinational Circuits


- ❖ Sequential Circuits

❖ Combinational Circuit

- ❖ $\text{Outputs} = F(\text{Inputs})$

- ❖ Function of Inputs only

- ❖ NO internal memory

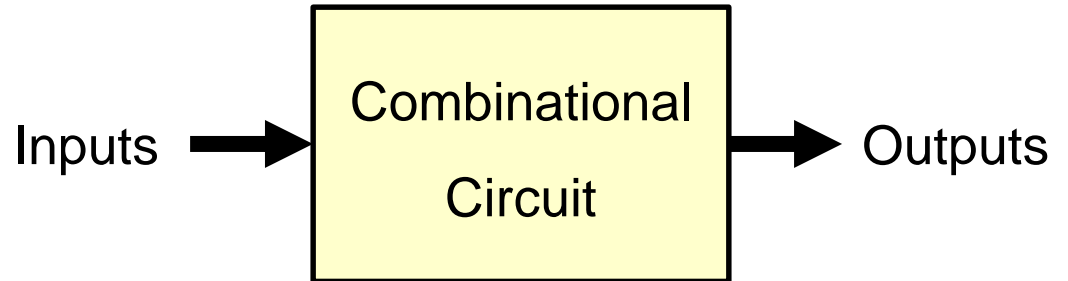

❖ Sequential Circuit

- ❖ Outputs is a function of Inputs and internal Memory

- ❖ There is an internal memory that stores the state of the circuit

- ❖ Time is very important: memory changes with time

Introduction to Sequential Circuits

A Sequential circuit consists of:

1. Memory elements:

- ✧ **Latches or Flip-Flops**
- ✧ Store the **Present State**


2. Combinational Logic

- ✧ Computes the **Outputs** of the circuit

Outputs depend on Inputs and Current State

- ✧ Computes the **Next State** of the circuit

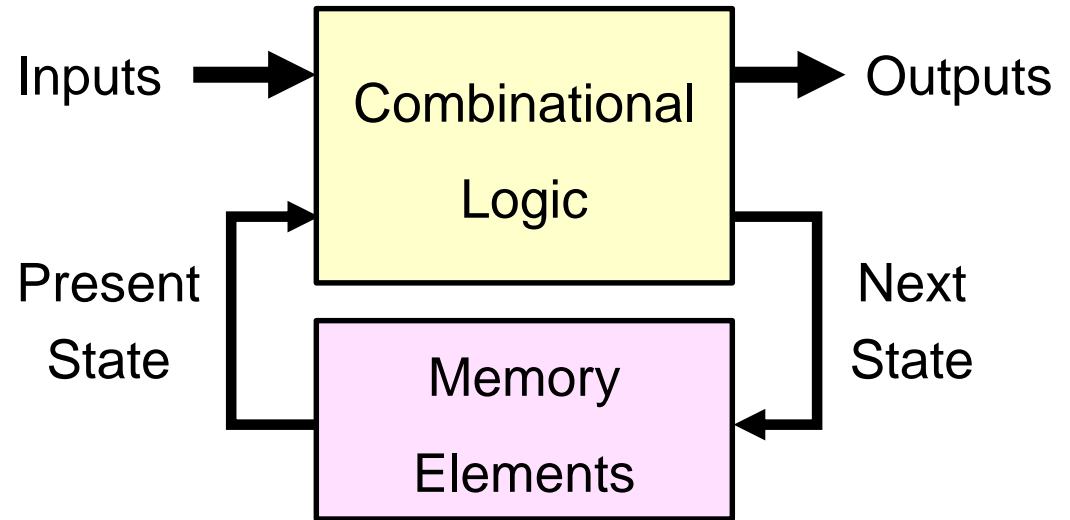Next State also depends on the Inputs and the Present State



Two Types of Sequential Circuits


1. **Synchronous** Sequential Circuit

- ✧ Uses a clock signal as an additional input
- ✧ Changes in the memory elements are controlled by the clock
- ✧ Changes happen at discrete instances of time

2. **Asynchronous** Sequential Circuit


- ✧ No clock signal
- ✧ Changes in the memory elements can happen at any instance of time
- ❖ Our focus will be on Synchronous Sequential Circuits
 - ✧ Easier to design and analyze than asynchronous sequential circuits

Synchronous Sequential Circuits

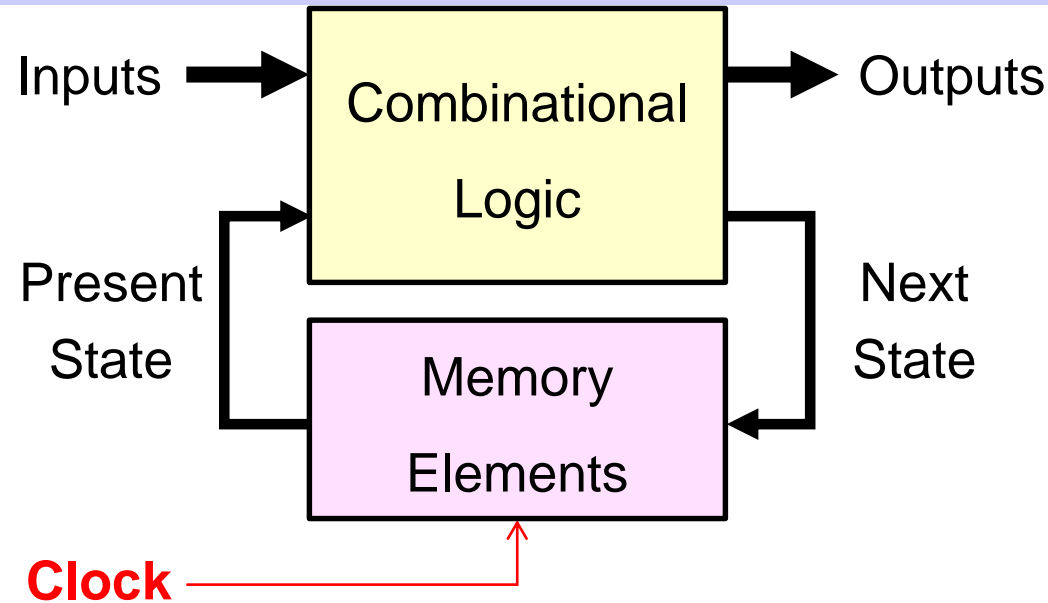


- ❖ Synchronous sequential circuits use a **clock signal**
- ❖ The clock signal is an input to the memory elements
- ❖ The clock determines **when** the memory should be updated
- ❖ The **present state** = output value of memory (stored)
- ❖ The **next state** = input value to memory (not stored yet)

The Clock

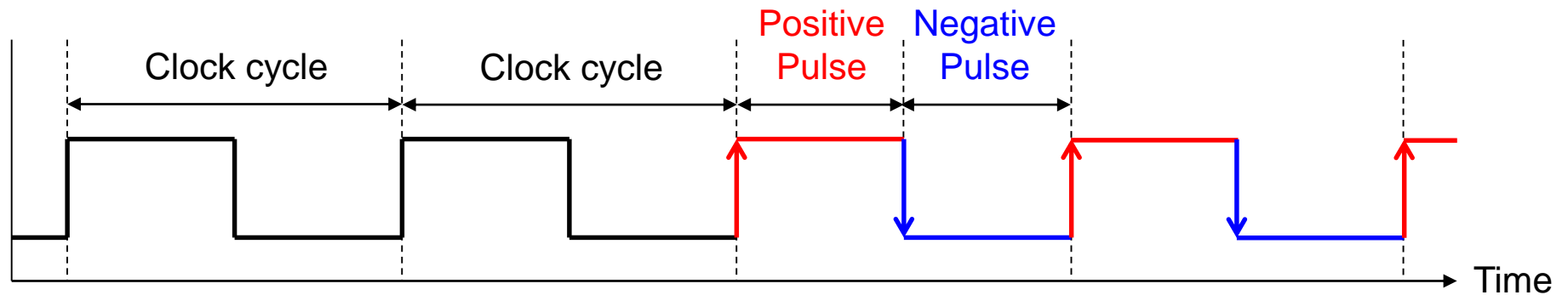

- ❖ Clock is a periodic signal = Train of pulses (1's and 0's)
- ❖ The same clock cycle repeats indefinitely over time(重复多次)
- ❖ **Positive Pulse**: when the **level** of the clock is **1**
- ❖ **Negative Pulse**: when the **level** of the clock is **0**
- ❖ **Rising Edge**: when the clock goes **from 0 to 1**
- ❖ **Falling Edge**: when the clock goes **from 1 down to 0**

Clock Cycle versus Clock Frequency

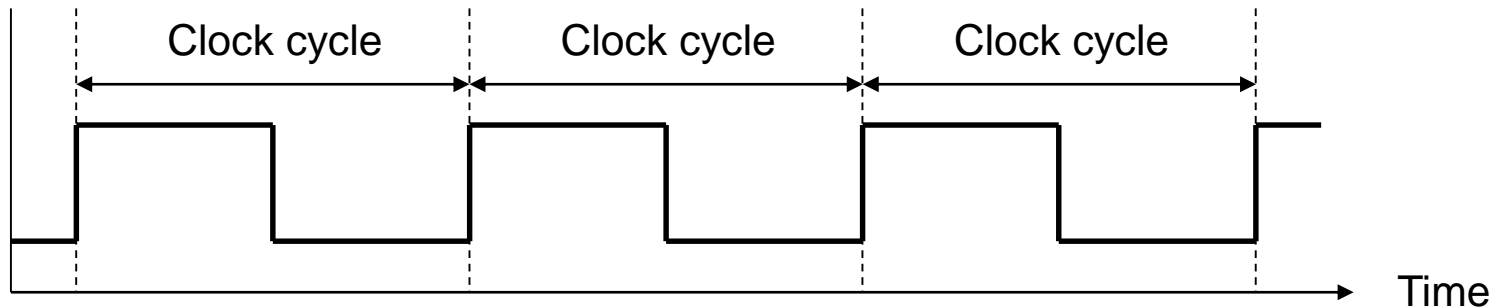

❖ Clock cycle (or period) is a time duration (时钟周期一段持续时间)

✧ Measured in seconds, milli-, micro-, nano-, or pico-seconds

✧ $1 \text{ ms} = 10^{-3} \text{ sec}$, $1 \mu\text{s} = 10^{-6} \text{ sec}$, $1 \text{ ns} = 10^{-9} \text{ sec}$, $1 \text{ ps} = 10^{-12} \text{ sec}$

❖ Clock frequency = number of cycles per second (Hertz)

✧ $1 \text{ Hz} = 1 \text{ cycle/sec}$, $1 \text{ kHz} = 10^3 \text{ Hz}$, $1 \text{ MHz} = 10^6 \text{ Hz}$, $1 \text{ GHz} = 10^9 \text{ Hz}$

❖ Clock frequency = $1 / \text{Clock Cycle}$

✧ Example: Given the clock cycle = $0.5 \text{ ns} = 0.5 \times 10^{-9} \text{ sec}$


✧ Then, the clock frequency = $1/(0.5 \times 10^{-9}) = 2 \times 10^9 \text{ Hz} = 2 \text{ GHz}$

Memory Elements

- ❖ Memory can store and maintain binary state (0's or 1's)
 - ✧ Until directed by an input signal to change state(直到被输入信号改变状态)
- ❖ Main difference between memory elements
 - ✧ Number of inputs they have(它们具有的输入个数)
 - ✧ How the inputs affect the binary state(输入如何影响二进制状态)
- ❖ Two main types:
 - ✧ **Latches** are level-sensitive (the level of the clock)
 - ✧ **Flip-Flops** are edge-sensitive (sensitive to the edge of the clock)
- ❖ Flip-Flops are used in synchronous sequential circuits
- ❖ Flip-Flops are built with latches

SR Latch

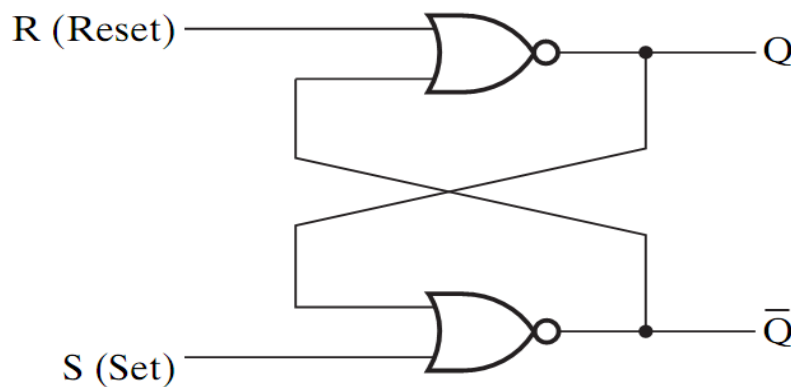- ❖ A **latch** is binary storage element that can store 0 or 1
- ❖ It is the most basic memory element
- ❖ An **SR Latch** can be built using two NOR gates
- ❖ Two inputs: S (Set) and R (Reset)
- ❖ Two outputs: Q and \bar{Q}




(a) Logic diagram

S	R	Q	\bar{Q}	
1	0	1	0	Set state
0	0	1	0	
0	1	0	1	Reset state
0	0	0	1	
1	1	0	0	Undefined

(b) Function table

SR Latch Operation

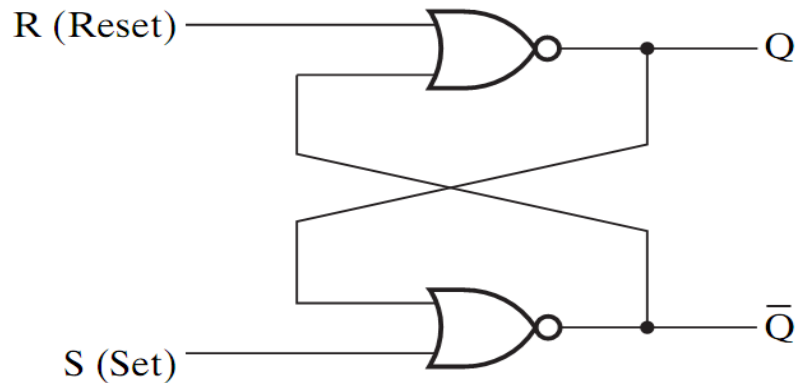


(a) Logic diagram

S	R	Q	\bar{Q}	
1	0	1	0	Set state
0	0	1	0	
0	1	0	1	Reset state
0	0	0	1	
1	1	0	0	Undefined

(b) Function table

- ❖ If $S = 1$ and $R = 0$ then **Set** ($Q = 1$, $\bar{Q} = 0$)
- ❖ If $S = 0$ and $R = 1$ then **Reset** ($Q = 0$, $\bar{Q} = 1$)
- ❖ When $S = R = 0$, Q and \bar{Q} are unchanged
- ❖ The latch stores its outputs Q and \bar{Q} as long as $S = R = 0$
- ❖ When $S = R = 1$, Q and \bar{Q} are undefined (should never be used)


SR Latch with NAND Gates

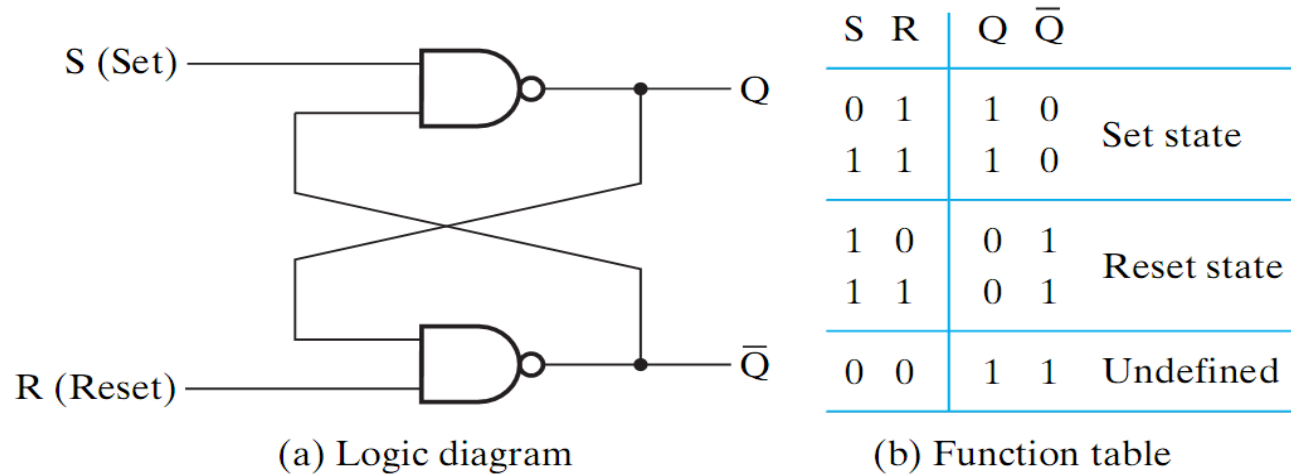

Known also
as $\bar{S} \bar{R}$ Latch

- ❖ If $S = 0$ and $R = 1$ then **Set** ($Q = 1$, $\bar{Q} = 0$)
- ❖ If $S = 1$ and $R = 0$ then **Reset** ($Q = 0$, $\bar{Q} = 1$)
- ❖ When $S = R = 1$, Q and \bar{Q} are unchanged (remain the same)
- ❖ The latch stores its outputs Q and \bar{Q} as long as $S = R = 1$
- ❖ When $S = R = 0$, Q and \bar{Q} are undefined (should never be used)

SR Latch with a Clock Input

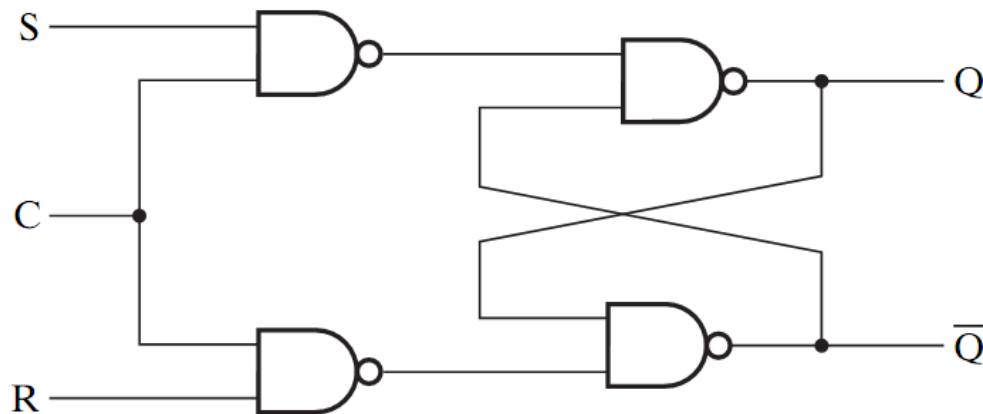

(a) Logic diagram

C	S	R	Next state of Q
0	X	X	No change
1	0	0	No change
1	0	1	Q = 0; Reset state
1	1	0	Q = 1; Set state
1	1	1	Undefined


(b) Function table

- ❖ An additional Clock input signal **C** is used
- ❖ Clock controls **when** the state of the latch can be changed
- ❖ When **C=0**, the S and R inputs have no effect on the latch

The latch will remain in the same state, regardless of S and R

- ❖ When **C=1**, then normal SR latch operation

D-Latch with a Clock Input

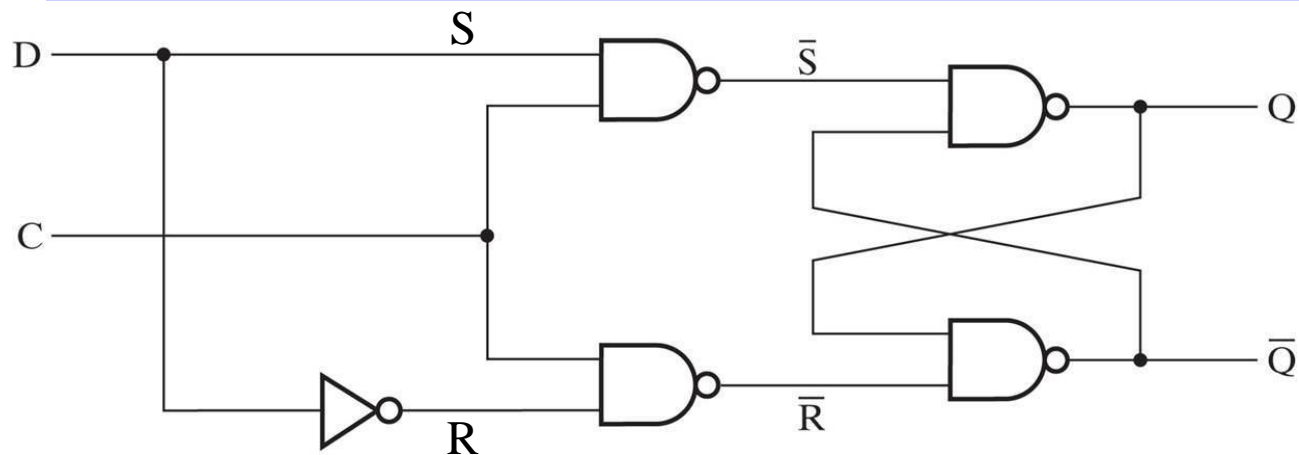


(a) Logic diagram

C	D	Next state of Q
0	X	No change
1	0	Q = 0; Reset state
1	1	Q = 1; Set state

(b) Function table

- ❖ Only one data input D
- ❖ An inverter is added: $S = D$ and $R = \bar{D}$
- ❖ S and R can never be 11 simultaneously → No undefined state
- ❖ When $C = 0$, Q remains the same (No change in state)
- ❖ When $C = 1$, $Q = D$ and $\bar{Q} = \bar{D}$

Graphic Symbols for Latches

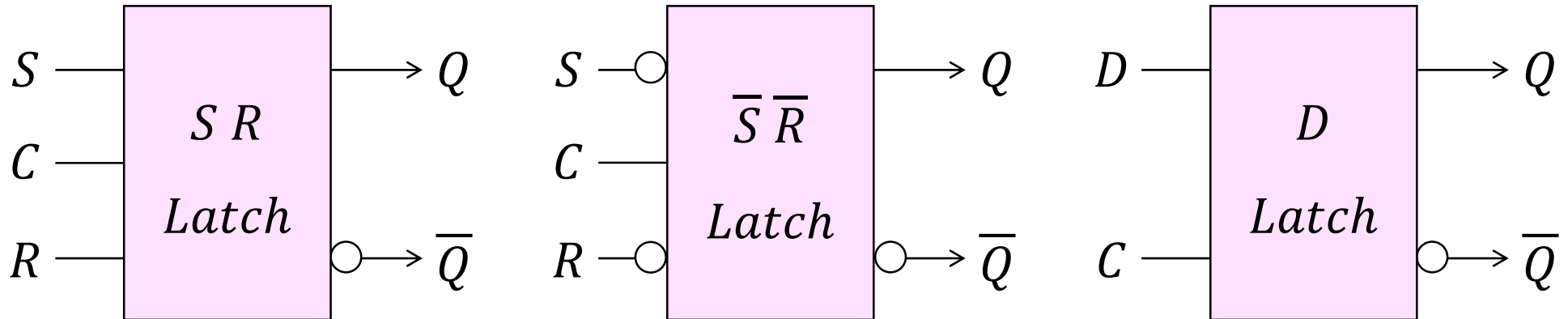

❖ A bubble appears at the complemented output \bar{Q}

Indicates that \bar{Q} is the complement of Q

❖ A bubble also appears at the inputs of an $\bar{S} \bar{R}$ latch

Indicates that **logic-0** is used (not logic-1) to set (or reset) the latch (as in the NAND latch implementation)


Problem with Latches

- ❖ A latch is **level-sensitive** (sensitive to the level of the clock)
- ❖ As long as the clock signal is **high** ...

Any change in the value of input D appears in the output Q


- ❖ Output Q keeps changing its value during a clock cycle (在一个时钟周期内，输出 Q 不断改变其值)
- ❖ Final value of output Q is uncertain

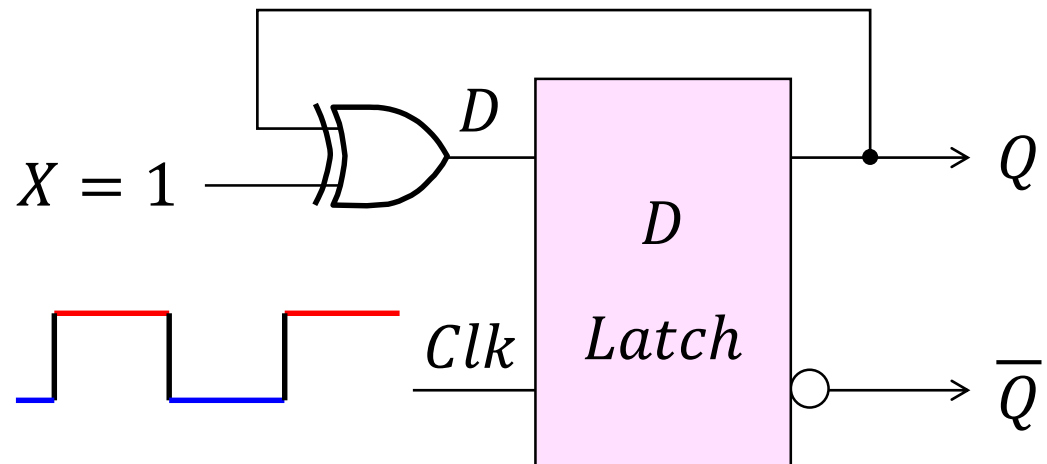Due to this uncertainty, latches are not used as memory elements in synchronous circuits



Flip-Flops

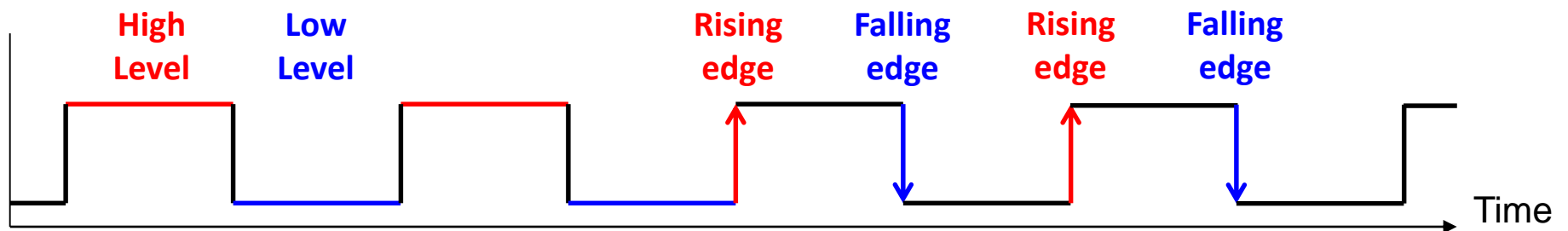- ❖ A **Flip-Flop** is a better memory element for synchronous circuits
- ❖ Solves the problem of latches in synchronous sequential circuits
- ❖ A **latch** is sensitive to the **level** of the clock
- ❖ However, a **flip-flop** is sensitive to the **edge** of the clock
- ❖ A flip-flop is called an **edge-triggered** memory element
- ❖ It changes its output value at the **edge** of the clock




Positive Edge-Triggered D Flip-Flop

- ❖ Built using two latches in a **master-slave** configuration
- ❖ A master latch (D-type) receives external inputs
- ❖ A slave latch (SR-type) receives inputs from the master latch
- ❖ Only one latch is enabled at any given time

When **C=0**, the master is enabled and the D input is latched (slave disabled)

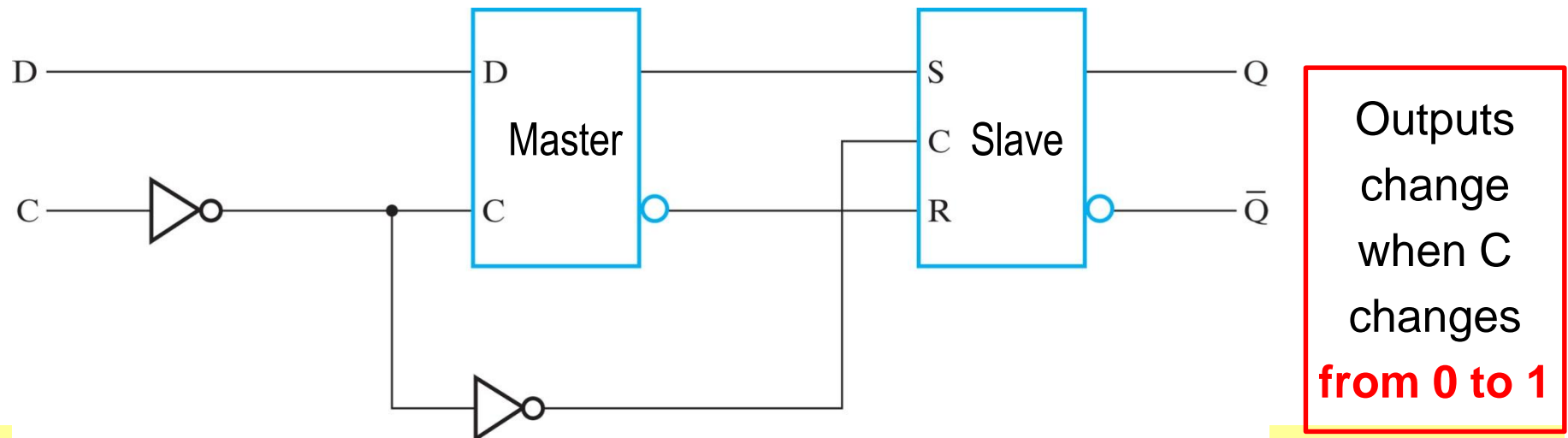When **C=1**, the slave is enabled to generate the outputs (master is disabled)




Negative Edge-Triggered D Flip-Flop

- ❖ Similar to positive edge-triggered flip-flop
- ❖ The first inverter at the Master C input is removed
- ❖ Only one latch is enabled at any given time

When **C=1**, the master is enabled and the D input is latched (slave disabled)

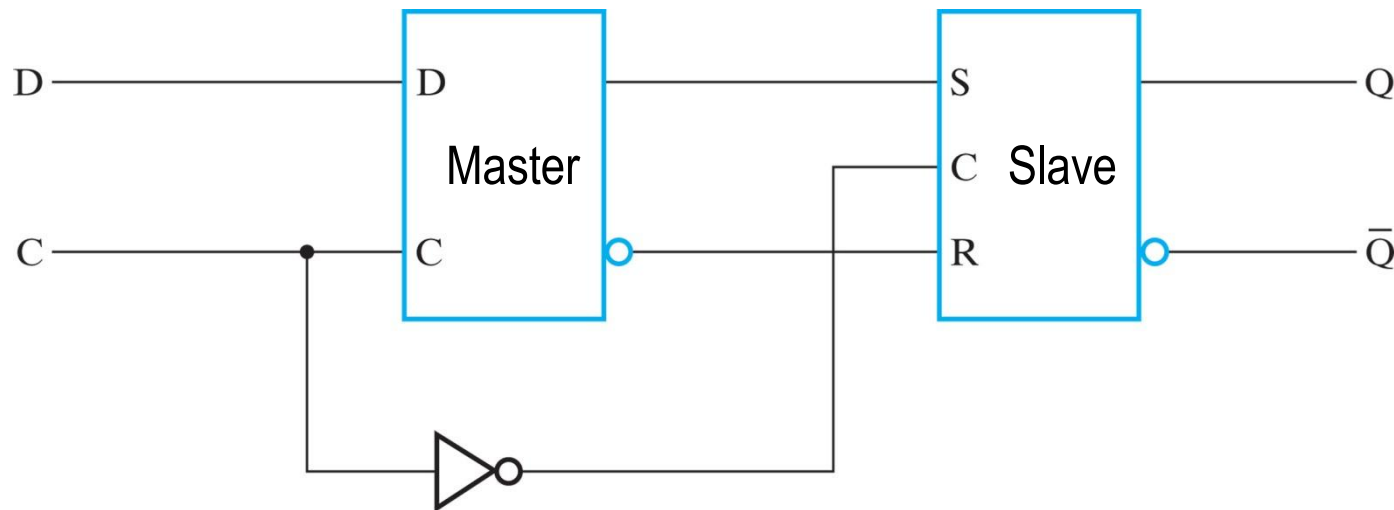
When **C=0**, the slave is enabled to generate the outputs (master is disabled)





Outputs
change
when C
changes
from 1 to 0

D Flip-Flop Timing Diagram

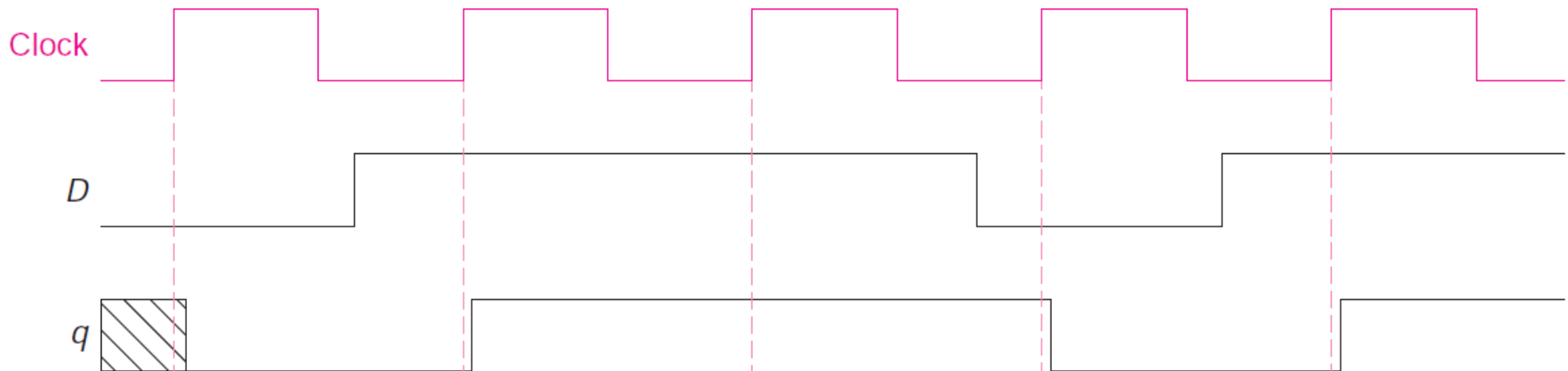- ❖ The diagram shows the timing of a positive edge D Flip-Flop
- ❖ The rising edge of the clock triggers the D Flip-Flop
- ❖ Initially, the value of q might be unknown
- ❖ Notice the slight delay in the output q (after the rising edge)




Graphic Symbols for Flip-Flops

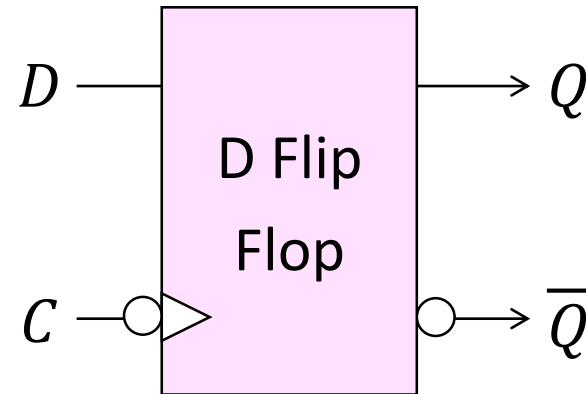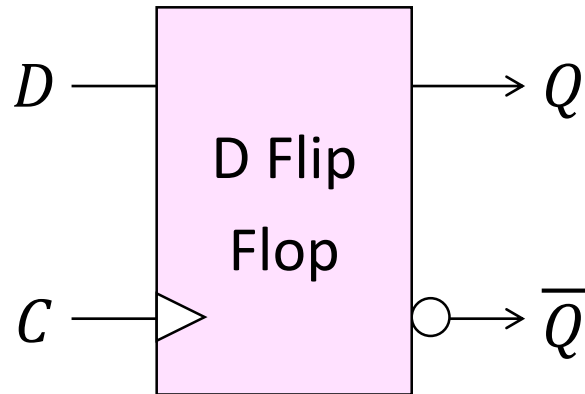

- ❖ A Flip-Flop has a similar symbol to a Latch
- ❖ The difference is the arrowhead at the clock input C
- ❖ The arrowhead indicates sensitivity to the edge of the clock
- ❖ A bubble at the C input indicates negative edge-triggered FF

D Flip-Flop with Asynchronous Reset

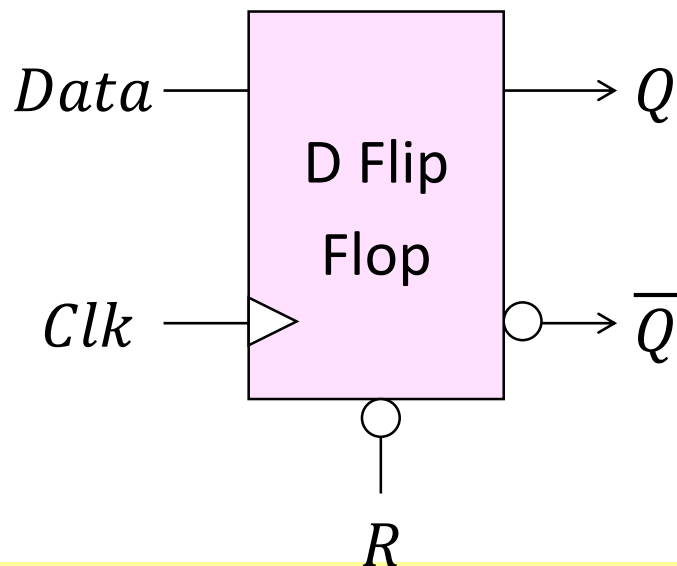- ❖ When Flip-Flops are powered, their initial state is unknown
- ❖ Some flip-flops have an **Asynchronous Reset** input R
- ❖ Resets the state (to logic value **0**), independent of the clock
- ❖ This is required to initialize a circuit before operation
- ❖ If the R input is inverted (bubble) then $R = 0$ resets the flip-flop




Inputs			Outputs	
R	$Data$	Clk	Q	\overline{Q}
0	X	X	0	1
1	0	↑	0	1
1	1	↑	1	0

Function Table


JK Flip-Flop

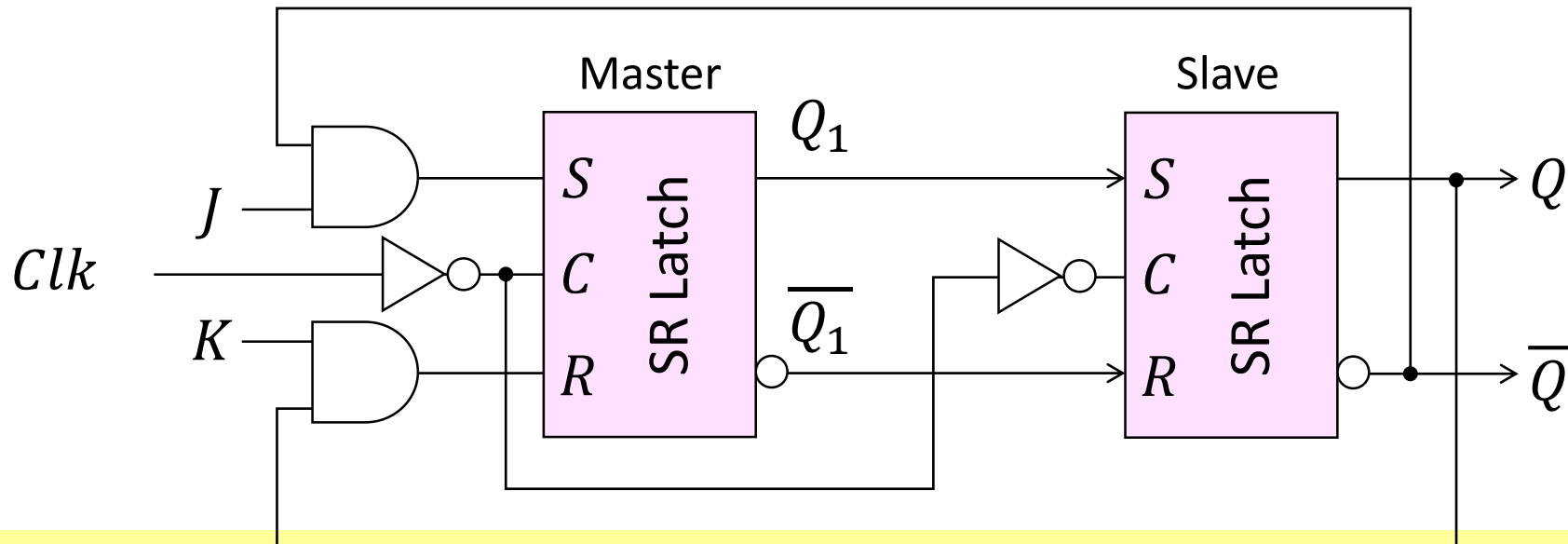- ❖ The *D* Flip-Flop is the most commonly used type
- ❖ The *JK* is another type of Flip-Flop with inputs: *J*, *K*, and *Clk*
- ❖ When $JK = 10 \rightarrow$ Set, When $JK = 01 \rightarrow$ Reset
- ❖ When $JK = 00 \rightarrow$ No change, When $JK = 11 \rightarrow$ Invert outputs
- ❖ *JK* can be implemented using two Clocked *SR* latches and gates




T Flip-Flop

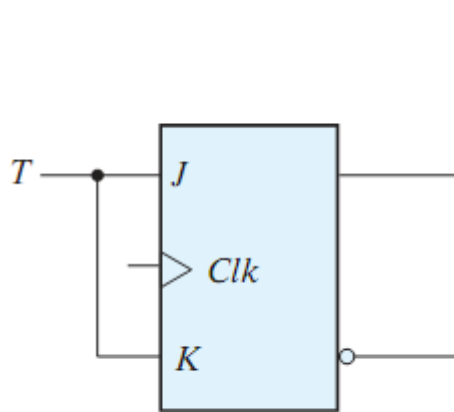
- ❖ The T (Toggle) flip-flop has inputs: T and Clk
- ❖ When $T = 0 \rightarrow$ No change, When $T = 1 \rightarrow$ Invert outputs
- ❖ The T flip-flop can be implemented using a JK flip-flop
- ❖ It can also be implemented using a D flip-flop and a XOR gate



(a) From JK flip-flop

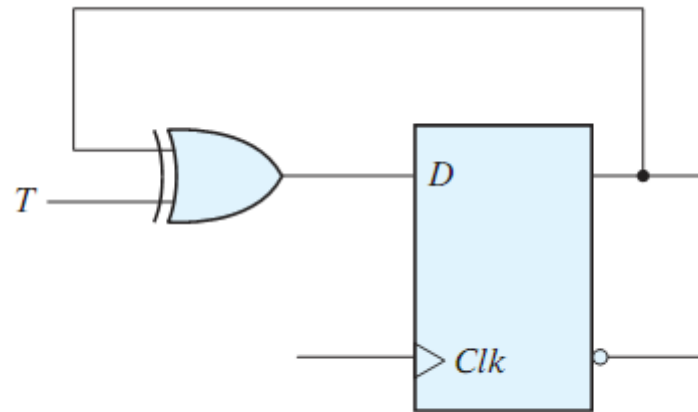

(b) From D flip-flop

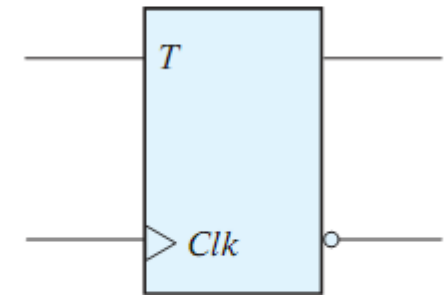

(c) Graphic symbol

Flip-Flop Characteristic Table

- ❖ Defines the operation of a flip-flop in a tabular form
- ❖ Next state is defined in terms of the current state and the inputs

$Q(t)$ refers to current state **before** the clock edge arrives

$Q(t + 1)$ refers to next state **after** the clock edge arrives

D Flip-Flop		
D	$Q(t+1)$	
0	0	Reset
1	1	Set

JK Flip-Flop			
J	K	$Q(t+1)$	
0	0	$Q(t)$	No change
0	1	0	Reset
1	0	1	Set
1	1	$Q'(t)$	Complement

T Flip-Flop		
T	$Q(t+1)$	
0	$Q(t)$	No change
1	$Q'(t)$	Complement

Flip-Flop Characteristic Equation

- ❖ The characteristic equation defines the operation of a flip-flop
- ❖ For D Flip-Flop: $Q(t + 1) = D$
- ❖ For JK Flip-Flop: $Q(t + 1) = J Q'(t) + K' Q(t)$
- ❖ For T Flip-Flop: $Q(t + 1) = T \oplus Q(t)$
- ❖ Clearly, the D Flip-Flop is the simplest among the three


D Flip-Flop	
D	$Q(t+1)$
0	0 Reset
1	1 Set

JK Flip-Flop	
$J \ K$	$Q(t+1)$
0 0	$Q(t)$ No change
0 1	0 Reset
1 0	1 Set
1 1	$Q'(t)$ Complement

T Flip-Flop	
T	$Q(t+1)$
0	$Q(t)$ No change
1	$Q'(t)$ Complement

Timing Considerations for Flip-Flops

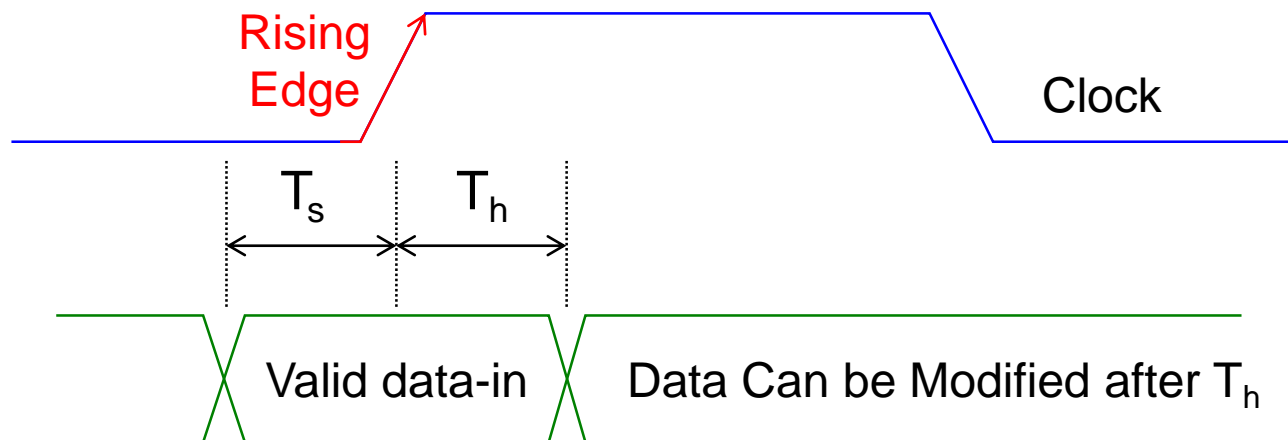- ❖ **Setup Time (T_s):** Time duration for which the data input must be valid and stable **before** the arrival of the clock edge.
- ❖ **Hold Time (T_h):** Time duration for which the data input must not be changed **after** the clock transition occurs.
- ❖ T_s and T_h must be ensured for the proper operation of flip-flops



Summary

- ❖ In a sequential circuit there is internal memory
 - ✧ Output is a function of current inputs and present state
 - ✧ The stored memory value defines the present state
 - ✧ Similarly, the next state depends on current inputs and present state
- ❖ Two types of sequential circuits:
 - ✧ Synchronous sequential circuits are clocked (easier to implement)
 - ✧ Asynchronous sequential circuits are not clocked
- ❖ Two types of Memory elements: Latches and Flip-Flops
- ❖ Latches are level-sensitive, flip-flops are edge-triggered
- ❖ Flip-flops are better memory elements for synchronous circuits
- ❖ A flip-flop is described using a characteristic table and equation