

Combinational logic circuits

EIC 0844091

Digital Circuit and Logic Design

Associate Prof. Luo Jie

Huazhong University of Science & Technology


Presentation Outline

- **Combinational logic circuits**
- **Logic circuit analysis**
- **Logic circuit design**

Combinational logic circuits

- ❑ Logic circuits are classified into two types, “combinational” and “sequential.”
- ❑ A combinational logic circuit is one whose outputs depend only on its current inputs.

 Structurally, there are no storage elements in combinational logic circuit.




Next topic

- **Combinational logic circuits**
- **Logic circuit analysis**
- **Logic circuit design**

Logic circuit analysis

□ Analysis

 The process to obtain the logic function of a logic circuit is called analysis.



The process usually includes following steps:


1. Derive the Boolean expressions of outputs from logic circuit.
2. Derive the truth table from Boolean expressions.
3. Determine the logic function according to truth table or Boolean expressions.

Logic circuit analysis

□ Analysis

 Example 1

A logic diagram is shown in figure. Determine its logic function.



Solution:

Boolean expressions

$$Z = A\bar{B} + \bar{A}B = A \oplus B$$


$$L = Z\bar{C} + \bar{Z}C = Z \oplus C = A \oplus B \oplus C$$

Truth table

Truth table				
<i>A</i>	<i>B</i>	<i>C</i>	<i>Z</i>	<i>L</i>
0	0	0	0	0
0	0	1	0	1
0	1	0	1	1
0	1	1	1	0
1	0	0	1	1
1	0	1	1	0
1	1	0	0	0
1	1	1	0	1

Logic circuit analysis

□ Analysis

 

Solution:

Boolean expressions

$$Z = A\bar{B} + \bar{A}B = A \oplus B$$

$$L = Z\bar{C} + \bar{Z}C = Z \oplus C = A \oplus B \oplus C$$

Truth table

Analyzing the logic function

When the number of 1s on the inputs is odd, the output L is 1. It is called 3-input odd parity checker.

Truth table

A	B	C	Z	L
0	0	0	0	0
0	0	1	0	1
0	1	0	1	1
0	1	1	1	0
1	0	0	1	1
1	0	1	1	0
1	1	0	0	0
1	1	1	0	1


How to construct a 4-input odd parity checker?

Logic circuit analysis

even parity output


How to construct a 4-input odd parity checker?

$$L = A \oplus B \oplus C$$

 

$$Y = A \oplus B \oplus C \oplus D$$
 
$$= (A \oplus B) \oplus (C \oplus D) = A \oplus (B \oplus C \oplus D)$$



How to construct a 4-input even parity checker?

Truth table

<i>ABCD</i>	<i>L</i>	<i>Y</i>	<i>W</i>
0 0 0 0	0	0	1
0 0 0 1	0	1	0
0 0 1 0	1	1	0
0 0 1 1	1	0	1
0 1 0 0	1	1	0
0 1 0 1	1	0	1
0 1 1 0	0	0	1
0 1 1 1	0	1	0
1 0 0 0	1	1	0
1 0 0 1	1	0	1
1 0 1 0	0	0	1
1 0 1 1	0	1	0
1 1 0 0	0	0	1
1 1 0 1	0	1	0
1 1 1 0	1	1	0
1 1 1 1	1	0	1

Logic circuit analysis


□ Analysis

Example 2

Determine the output waveform X for the logic circuit in figure, with input waveforms A and B as shown.

Solution:

Marking intermediate variables


 


$$X = AB + \bar{A}\bar{B}$$

XNOR
operation

Note:

 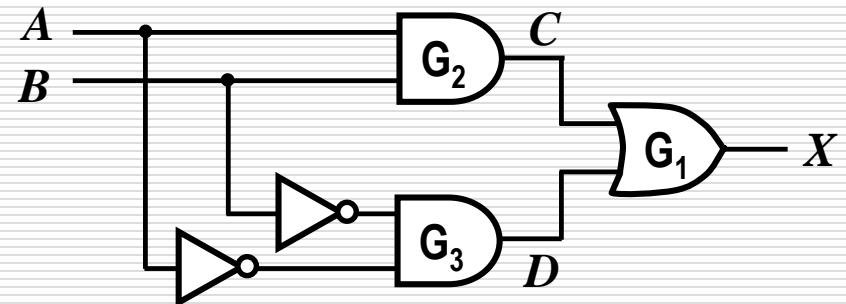Ignoring the transition time and propagation delay usually when analyzing only logic function unless otherwise stated.




Next topic

- **Combinational logic circuits**
- **Logic circuit analysis**
- **Logic circuit design**

Logic circuit design

□ Design

 The process to implement the logic function using a certain logic circuit is called design.



The process usually includes following steps:

1. From the specification of the logic function, determine the required number of inputs and outputs and assign a symbol to each.
2. Derive the truth table that defines the required relationship between inputs and outputs.
3. Obtain the simplified Boolean expressions for each output.
4. Draw the logic diagram.

Logic circuit design

□ Design

Example 1

Design a logic circuit for converting BCD code to Excess-3 code.

Solution:

Inputs: A_3, A_2, A_1, A_0

Outputs: Y_3, Y_2, Y_1, Y_0

Truth table

Using K-Map to simplify the function for each output

Dec	$A_3A_2A_1A_0$	$Y_3Y_2Y_1Y_0$
0	0 0 0 0	0 0 1 1
1	0 0 0 1	0 1 0 0
2	0 0 1 0	0 1 0 1
3	0 0 1 1	0 1 1 0
4	0 1 0 0	0 1 1 1
5	0 1 0 1	1 0 0 0
6	0 1 1 0	1 0 0 1
7	0 1 1 1	1 0 1 0
8	1 0 0 0	1 0 1 1
9	1 0 0 1	1 1 0 0
10	1 0 1 0	x x x x
11	1 0 1 1	x x x x
12	1 1 0 0	x x x x
13	1 1 0 1	x x x x
14	1 1 1 0	x x x x
15	1 1 1 1	x x x x

Design examples

Using K-Map to simplify the function for each output

Y_0		A_1A_0			
A_3A_2		00	01	11	10
00	1				1
01	1				1
11	x	x	x	x	x
10	1		x		x

$A_3A_2A_1A_0$	$Y_3Y_2Y_1Y_0$
0 0 0 0	0 0 1 1
0 0 0 1	0 1 0 0
0 0 1 0	0 1 0 1
0 0 1 1	0 1 1 0
0 1 0 0	0 1 1 1
0 1 0 1	1 0 0 0
0 1 1 0	1 0 0 1
0 1 1 1	1 0 1 0
1 0 0 0	1 0 1 1
1 0 0 1	1 1 0 0
1 0 1 0	x x x x
1 0 1 1	x x x x
1 1 0 0	x x x x
1 1 0 1	x x x x
1 1 1 0	x x x x
1 1 1 1	x x x x

Design examples

Using K-Map to simplify the function for each output

Y_0 $A_1 A_0$

$A_3 A_2$	00	01	11	10
00	1			1
01	1			1
11	x	x	x	x
10	1		x	x

Y_1 $A_1 A_0$

$A_3 A_2$	00	01	11	10
00	1		1	
01	1		1	
11	x	x	x	x
10	1		x	x

Y_2 $A_1 A_0$

$A_3 A_2$	00	01	11	10
00		1	1	1
01	1			
11	x	x	x	x
10		1	x	x

Y_3 $A_1 A_0$

$A_3 A_2$	00	01	11	10
00				
01		1	1	1
11	x	x	x	x
10	1	1	x	x

$$Y_0 = \bar{A}_0$$

$$Y_1 = \bar{A}_1 \bar{A}_0 + A_1 A_0$$

$$Y_2 = \bar{A}_2 A_0 + \bar{A}_2 A_1 + A_2 \bar{A}_1 \bar{A}_0$$

$$Y_3 = A_3 + A_2 A_0 + A_2 A_1$$

$A_3 A_2 A_1 A_0$	$Y_3 Y_2 Y_1 Y_0$
0 0 0 0	0 0 1 1
0 0 0 1	0 1 0 0
0 0 1 0	0 1 0 1
0 0 1 1	0 1 1 0
0 1 0 0	0 1 1 1
0 1 0 1	1 0 0 0
0 1 1 0	1 0 0 1
0 1 1 1	1 0 1 0
1 0 0 0	1 0 1 1
1 0 0 1	1 1 0 0
1 0 1 0	x x x x
1 0 1 1	x x x x
1 1 0 0	x x x x
1 1 0 1	x x x x
1 1 1 0	x x x x
1 1 1 1	x x x x

Design examples

The logic diagram

$$Y_0 = \bar{A}_0$$

$$Y_1 = \bar{A}_1\bar{A}_0 + A_1A_0$$

$$Y_2 = \bar{A}_2A_0 + \bar{A}_2A_1 + A_2\bar{A}_1\bar{A}_0$$

$$Y_3 = A_3 + A_2A_0 + A_2A_1$$

Transformation

$$Y_0 = \bar{A}_0$$

$$Y_1 = \bar{A}_1\bar{A}_0 + A_1A_0$$

$$= \overline{A_1 + A_0} + A_1A_0$$

$$Y_2 = \bar{A}_2A_0 + \bar{A}_2A_1 + A_2\bar{A}_1\bar{A}_0$$

$$= \bar{A}_2(A_1 + A_0) + A_2\overline{(A_1 + A_0)}$$


$$Y_3 = A_3 + A_2A_0 + A_2A_1$$

$$= A_3 + A_2(A_1 + A_0)$$

Note:

when the circuit have more than one output, the common parts in output expressions are more, the final circuit is more simpler.

 In this case, we hope the expressions contain most possible common parts.



Logic circuit design

□ Design

Example 2

Design a logic circuit for converting Gray code to binary code.

Solution:

Inputs: G_3, G_2, G_1, G_0

Outputs: B_3, B_2, B_1, B_0

Truth table

Binary $B_3B_2B_1B_0$	Gray $G_3G_2G_1G_0$
0 0 0 0	0 0 0 0
0 0 0 1	0 0 0 1
0 0 1 0	0 0 1 1
0 0 1 1	0 0 1 0
0 1 0 0	0 1 1 0
0 1 0 1	0 1 1 1
0 1 1 0	0 1 0 1
0 1 1 1	0 1 0 0
1 0 0 0	1 1 0 0
1 0 0 1	1 1 0 1
1 0 1 0	1 1 1 1
1 0 1 1	1 1 1 0
1 1 0 0	1 0 1 0
1 1 0 1	1 0 1 1
1 1 1 0	1 0 0 1
1 1 1 1	1 0 0 0

Logic circuit design

□ Design

Example 2

Design a logic circuit for converting Gray code to binary code.

Solution:

Inputs: G_3, G_2, G_1, G_0

Outputs: B_3, B_2, B_1, B_0

Truth table

Using K-Map to simplify the function for each output

Input	Output
Gray	Binary
$G_3G_2G_1G_0$	$B_3B_2B_1B_0$
0 0 0 0	0 0 0 0
0 0 0 1	0 0 0 1
0 0 1 1	0 0 1 0
0 0 1 0	0 0 1 1
0 1 1 0	0 1 0 0
0 1 1 1	0 1 0 1
0 1 0 1	0 1 1 0
0 1 0 0	0 1 1 1
1 1 0 0	1 0 0 0
1 1 0 1	1 0 0 1
1 1 1 1	1 0 1 0
1 1 1 0	1 0 1 1
1 0 1 0	1 1 0 0
1 0 1 1	1 1 0 1
1 0 0 1	1 1 1 0
1 0 0 0	1 1 1 1

Design examples

Using K-Map to simplify the function for each output

B_0		G_1G_0			
G_3G_2		00	01	11	10
00			1		1
01		1		1	
11			1		1
10		1		1	

Input	Output
Gray	Binary
$G_3G_2G_1G_0$	$B_3B_2B_1B_0$
0 0 0 0	0 0 0 0
0 0 0 1	0 0 0 1
0 0 1 1	0 0 1 0
0 0 1 0	0 0 1 1
0 1 1 0	0 1 0 0
0 1 1 1	0 1 0 1
0 1 0 1	0 1 1 0
0 1 0 0	0 1 1 1
1 1 0 0	1 0 0 0
1 1 0 1	1 0 0 1
1 1 1 1	1 0 1 0
1 1 1 0	1 0 1 1
1 0 1 0	1 1 0 0
1 0 1 1	1 1 0 1
1 0 0 1	1 1 1 0
1 0 0 0	1 1 1 1

Design examples

Using K-Map to simplify the function for each output

B_0 G_1G_0

G_3G_2	00	01	11	10
00		1		1
01	1		1	
11		1		1
10	1		1	

B_1 G_1G_0

G_3G_2	00	01	11	10
00			1	1
01	1	1		
11			1	1
10	1	1		

B_2 G_1G_0

G_3G_2	00	01	11	10
00				
01	1	1	1	1
11				
10	1	1	1	1

B_3 G_1G_0

G_3G_2	00	01	11	10
00				
01				
11	1	1	1	1
10	1	1	1	1

$$B_3 = G_3$$

$$B_2 = \overline{G_3}G_2 + G_3\overline{G_2}$$

$$B_1 = G_3\overline{G_2}\overline{G_1} + G_3G_2G_1 + \overline{G_3}G_2\overline{G_1} + \overline{G_3}\overline{G_2}G_1$$

$$B_0 = G_3 \oplus G_2 \oplus G_1 \oplus G_0$$

Input	Output
Gray	Binary
$G_3G_2G_1G_0$	$B_3B_2B_1B_0$
0 0 0 0	0 0 0 0
0 0 0 1	0 0 0 1
0 0 1 1	0 0 1 0
0 0 1 0	0 0 1 1
0 1 1 0	0 1 0 0
0 1 1 1	0 1 0 1
0 1 0 1	0 1 1 0
0 1 0 0	0 1 1 1
1 1 0 0	1 0 0 0
1 1 0 1	1 0 0 1
1 1 1 1	1 0 1 0
1 1 1 0	1 0 1 1
1 0 1 0	1 1 0 0
1 0 1 1	1 1 0 1
1 0 0 1	1 1 1 0
1 0 0 0	1 1 1 1

Design examples

The logic diagram

$$B_3 = G_3 \quad B_2 = \overline{G_3}G_2 + G_3\overline{G_2}$$

$$B_1 = G_3\overline{G_2}\overline{G_1} + G_3G_2G_1 + \overline{G_3}G_2\overline{G_1} + \overline{G_3}\overline{G_2}G_1$$

$$B_0 = G_3 \oplus G_2 \oplus G_1 \oplus G_0$$

Transformation

$$B_3 = G_3$$

$$B_2 = \overline{G_3}G_2 + G_3\overline{G_2} = G_3 \oplus G_2$$


$$B_1 = G_3\overline{G_2}\overline{G_1} + G_3G_2G_1 + \overline{G_3}G_2\overline{G_1} + \overline{G_3}\overline{G_2}G_1$$

$$= (G_3\overline{G_2} + \overline{G_3}G_2)\overline{G_1} + (G_3G_2 + \overline{G_3}\overline{G_2})G_1$$

$$= (G_3 \oplus G_2)\overline{G_1} + \overline{(G_3 \oplus G_2)}G_1$$

$$= G_3 \oplus G_2 \oplus G_1 = B_2 \oplus G_1$$
 
$$B_0 = G_3 \oplus G_2 \oplus G_1 \oplus G_0 = B_1 \oplus G_0$$




Design examples

□ Example 3

A water tank supply is shown in figure. The feed-tank are supplied with water by two water pumps L_1 and L_2 . A , B and C represent three water level detecting elements respectively. When the water level is above their position on the feed-tank, the outputs of them are LOW. When the water level is below their position, the outputs of them are HIGH.

Design a logic circuit to control water pumps L_1 and L_2 . It is required:

 
1. When the level is above the position of C , both L_1 and L_2 are stopping.
2. When the level is above the position of B and below the position of C , only L_1 is running.
3. When the level is above A and below B , only L_2 is running.
4. When the level is below A , both L_1 and L_2 are running.



Design examples

Solution:

Definition

 

Inputs: A, B, C


A, B and C indicate output of detecting elements respectively

Each of them is 0 if water level is above it, and it is 1 if water level is below it.


Outputs: L_2, L_1

When each of them is 1,
the corresponding pump is running.

 When each of them is 0,
the corresponding the pump is stopping.



Design examples

 

Solution: Inputs: A, B, C

It is 0 if water level is above it.

It is 1 if water level is below it.

Outputs: L_2, L_1

It is 1, the corresponding pump is running.

It is 0, the corresponding the pump is stopping.

Truth table

It is required:

1. When the level is above the position of C , both L_1 and L_2 are stopping.
2. When the level is above the position of B and below the position of C , only L_1 is running.
3. When the level is above A and below B , only L_2 is running.
4. When the level is below A , both L_1 and L_2 are running.

Truth table

A	B	C	L_2	L_1
0	0	0	0	0
0	0	1	0	1
0	1	0	x	x
0	1	1	1	0
1	0	0	x	x
1	0	1	x	x
1	1	0	x	x
1	1	1	1	1

Four states never occur

Design examples

Solution:

The expressions and simplification

L_1

$AB \backslash C$	0	1
00		1
01	x	
11	x	1
10	x	x

$$L_1 = A + \bar{B}C$$

L_2


$AB \backslash C$	0	1
00		
01	x	1
11	x	1
10	x	x

$$L_2 = B$$

Truth table

A	B	C	L_2	L_1
0	0	0	0	0
0	0	1	0	1
0	1	0	x	x
0	1	1	1	0
1	0	0	x	x
1	0	1	x	x
1	1	0	x	x
1	1	1	1	1

The logic diagram

 

Design examples

□ Example 4

Given the input and output waveforms in figure. Design a logic circuit to implement the logic relationship between inputs and output.

Solution:


*Construct the truth table
from waveforms*

Truth table

<i>C</i>	<i>B</i>	<i>A</i>	<i>X</i>
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

*The expressions and
simplification*

$$X = CA + \overline{B}C$$

 

The logic diagram


(skipped)

<i>CB</i>	<i>A</i>	<i>X</i>
00	0	1
01	1	0
11	0	1
10	1	1

Design examples

□ Example 4

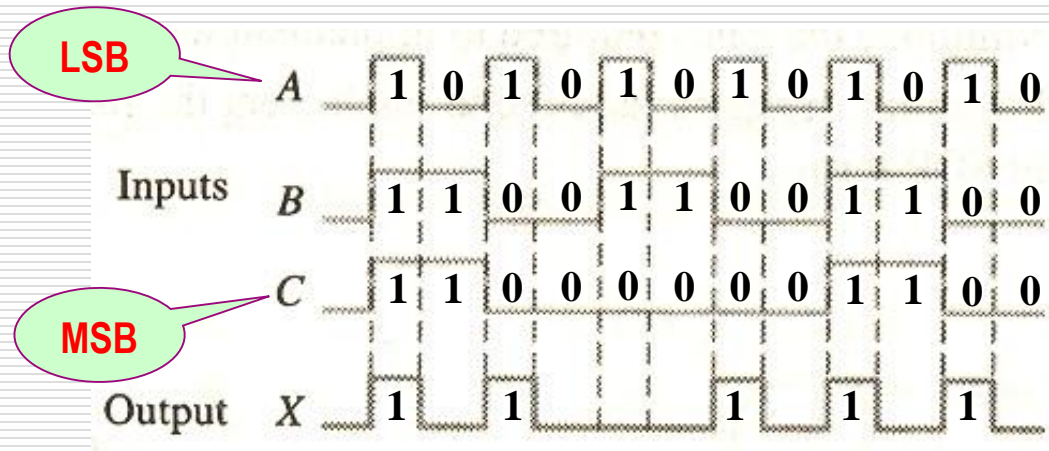What is its truth table if the waveforms are shown in figure ?



Truth table			
C	B	A	X
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	x
1	0	1	x
1	1	0	0
1	1	1	1

For the combinations of inputs those don't appear in waveforms corresponding outputs are filled with 'x'.